

Measuring Current

- There is a greater potential for meter damage when measuring current than with any other function.
- Just as in voltage, there are two kinds of current associated with the voltage, AC and DC.
- This meter will only measure DC current, more expensive meters will measure both currents.
- To measure current, the **VOM must be inserted *into the circuit*** so that the current flows ***through*** the meter.

Measuring Current

- There are two current ranges, high – up to 10 amps, and low – 200 milliamps (0.2 amps) and below.
- Internal fuses provide some meter protection for over current situations.
 - Because there is such a wide range between the current scales, there are two physical probe jacks for the two ranges
 - This allows for better protection, a hardy fuse to handle up to 10 amps of current and a more fragile fuse to protect the sensitive circuits needed to measure small currents.
 - Don't count on the fuses to protect the meter!


Measuring Current

- **CAUTION!!!!!!!** There must be some resistance in the circuit or the current flow through the circuit will be the maximum the source will produce, **AND THIS CURRENT LEVEL COULD DAMAGE THE VOM!**
- In other words, **DO NOT CONNECT THE VOM PROBES DIRECTLY ACROSS THE BATTERY POLES IN THE CURRENT MEASUREMENT FUNCTION!**


Measuring Current

- We will be demonstrating some concepts during the current measurement exercises that will be covered in more detail later, so be patient, it will all come together in the end.
- In the following exercises you will use various resistors to limit the current flow in a simple circuit.

The Proto Board

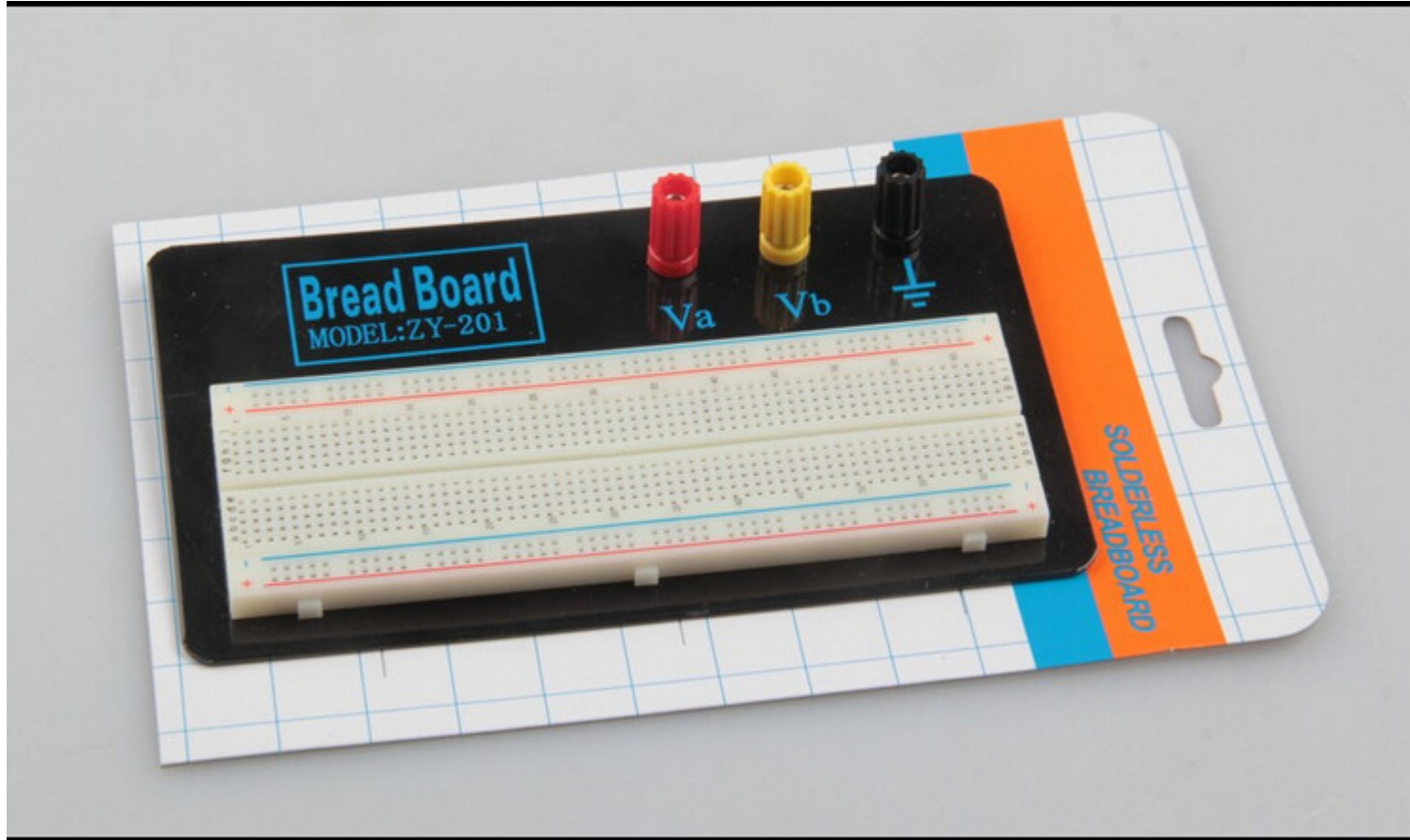


Measuring Current Basic Circuit

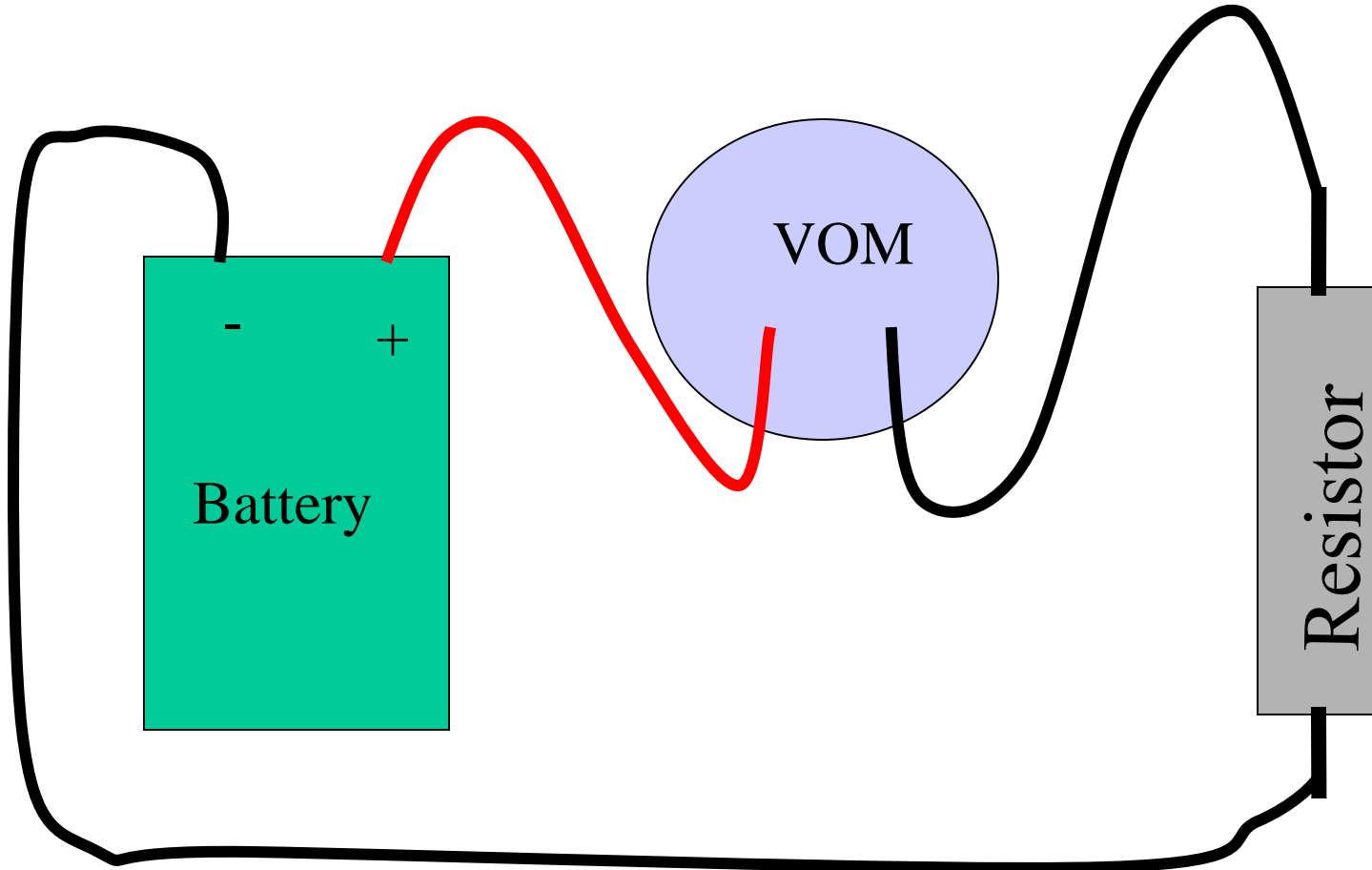


First Current Measurement

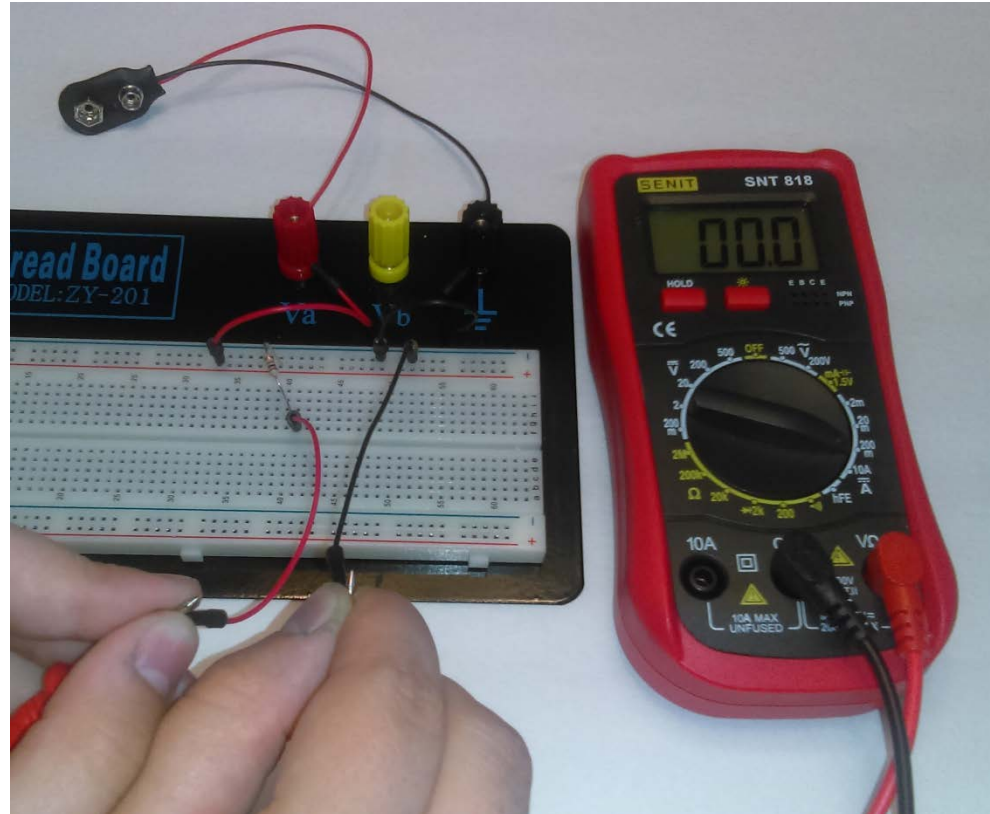- Set up the circuit using a 100 ohm resistor (brown, black, brown).
- Connect a wire to the + power source, connect another wire to the top end of the resistor (the non grounded end).
- Set VOM current scale to 200 m. (m here is short for mA)
- Without connecting the battery, practice touching the VOM probes to the exposed wire ends.




First Current Measurement

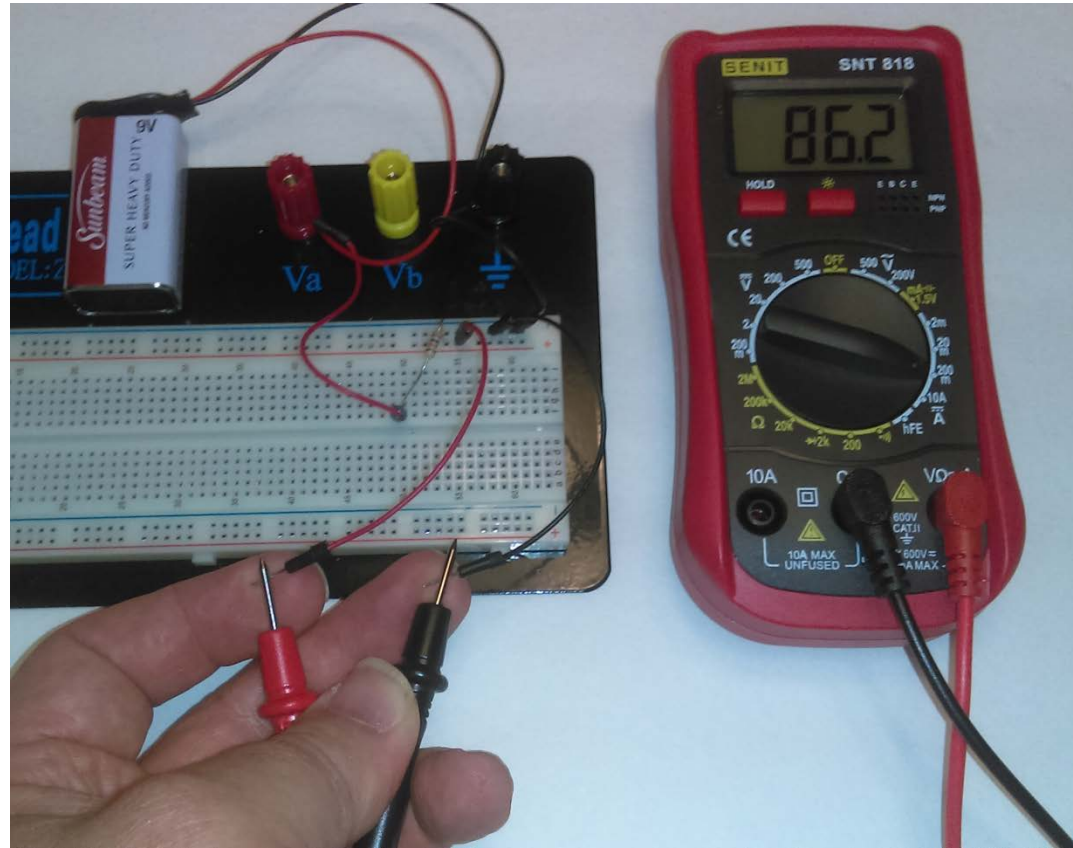- Connect the battery.
- With the VOM set to the 200 m current scale, touch the black lead to the wire hooked to the top side of the resistor.
- Touch the red lead to the lead coming from the + side of the battery.
- Note the VOM reading.




First Current Measurement

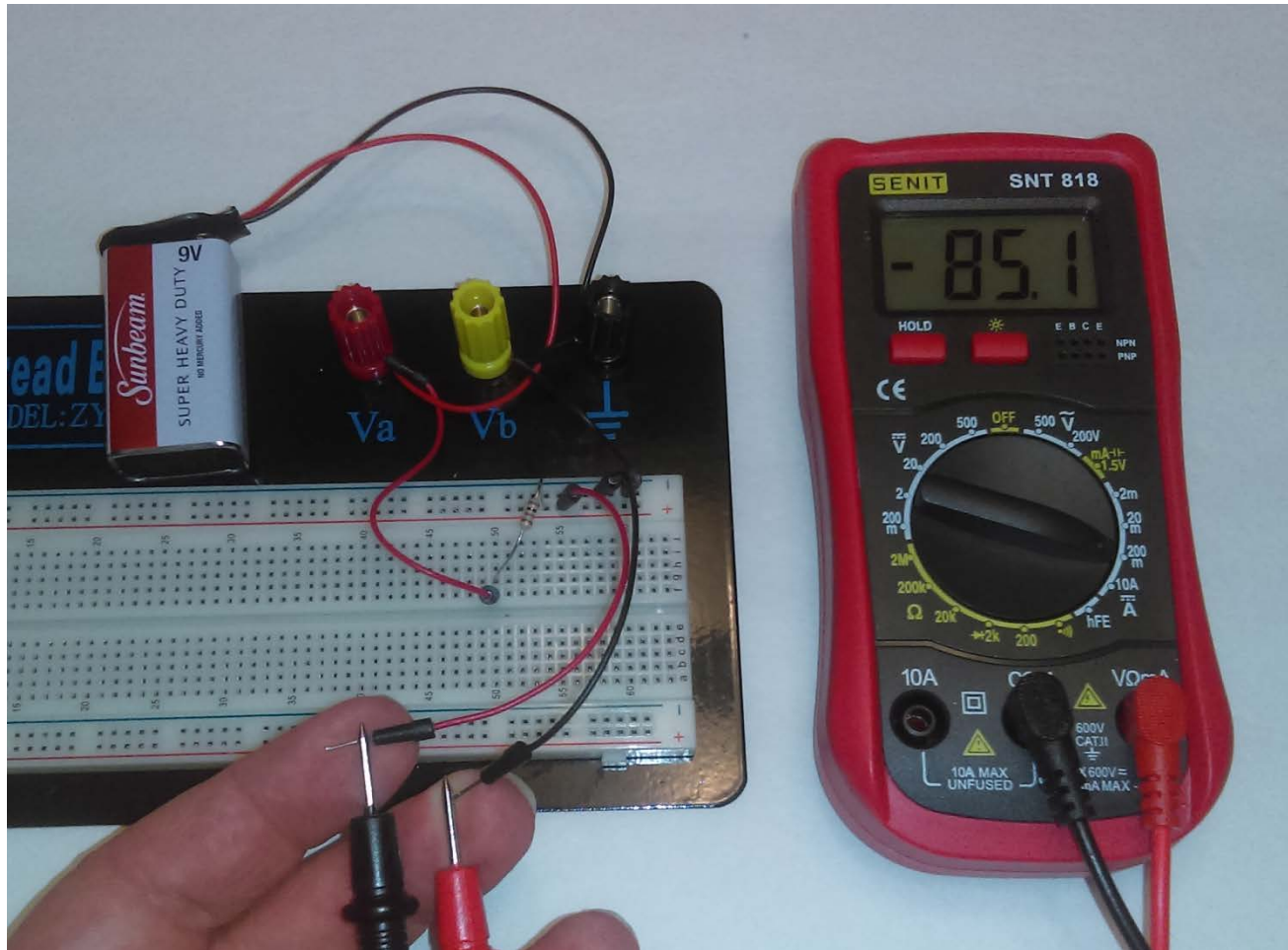


- Now reverse the VOM leads and note the reading.

First Current Measurement

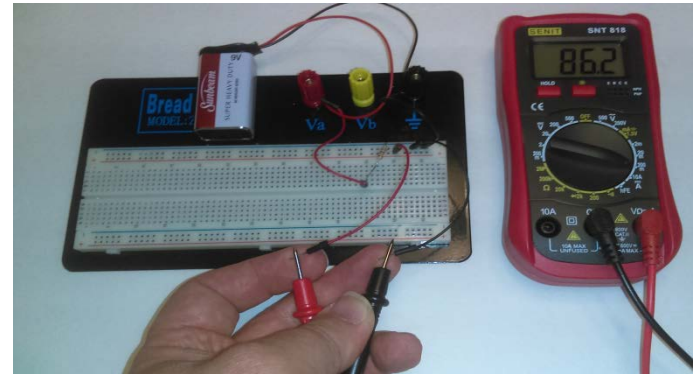- Return the VOM leads so that the **red** is connected to the battery.
- Change the VOM current ranges down and note the display readings
- What is the best range for measuring the current from a 9 volt source through a 100 ohm resistor?



200 m Range

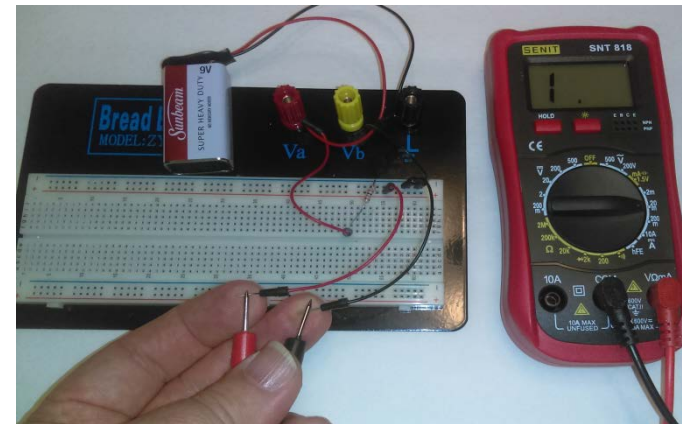

20 m Range